
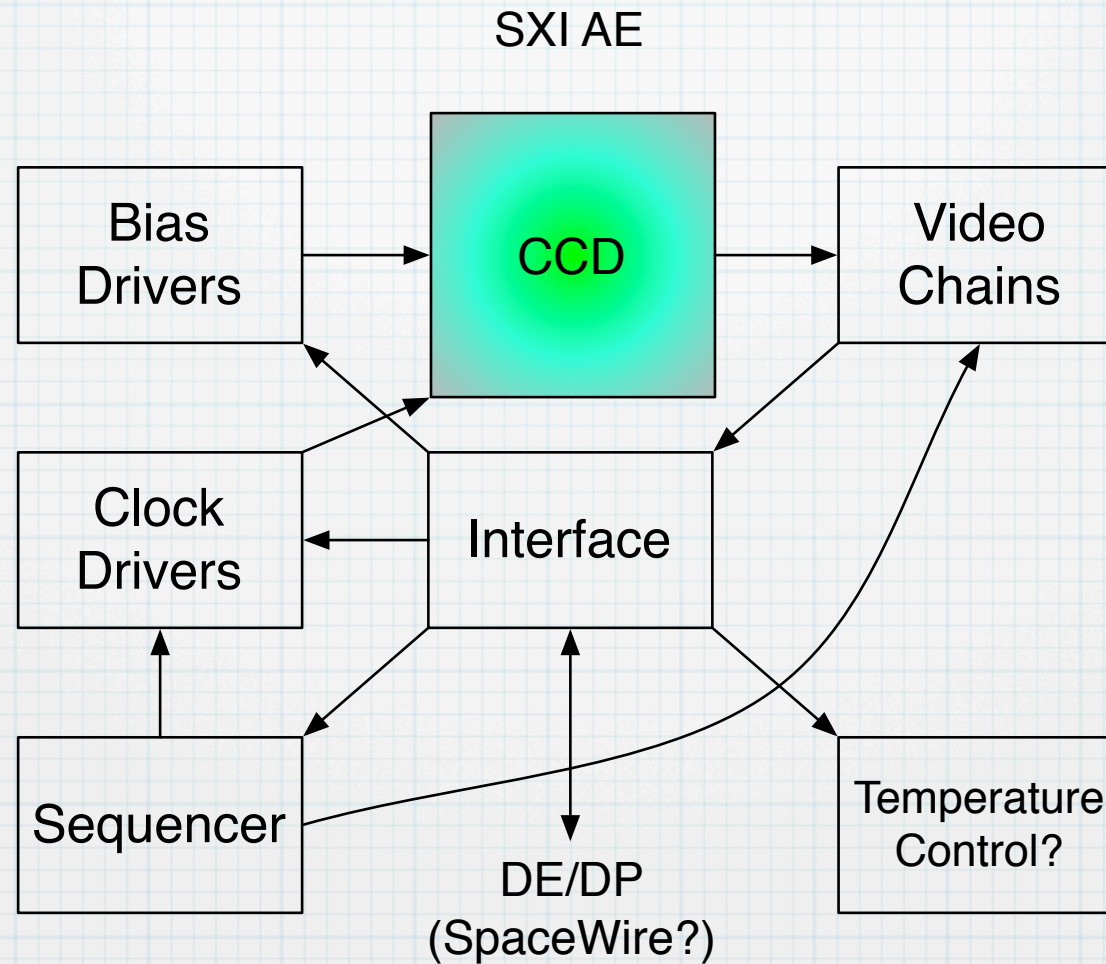


 SXI Electronics Development at Noqsi Aerospace





Design Practices

Use ISAS style.

Be conservative but not dogmatic.


Protect against CMOS SEL with current limits.

Protect against SEU operationally with periodic resets and reinitialization.

Avionics parts when possible.

Meet needs of instrument first.

 Assume instrument receives regulated (“2ry”) power.



Clock Drivers

Requirements:

± 15 V max swing

(large)

1MHz pixel rate

(for serials: what about parallel clocks?)


Parts procurable in Japan

Handle two phase CCD's up to 25 cm²

Goals:

Low power

High reliability

 

Design Parameters

Capacitances?

Guess 75 nF for each parallel phase.


Guess 200 pF (including cable) for each serial phase and reset clock.

How much peak power available for parallel clocks?

Assume radiation environment similar to ASCA and Suzaku.

Moderate dose.

SEU likely. SEL possible.


 


Low capacitance drivers (serial and reset)


Noqsi Aerospace, Ltd.

2822 South Nova Road, Pine, Colorado, USA 80470


+1-303-816-2756 jpd@wispartel.net

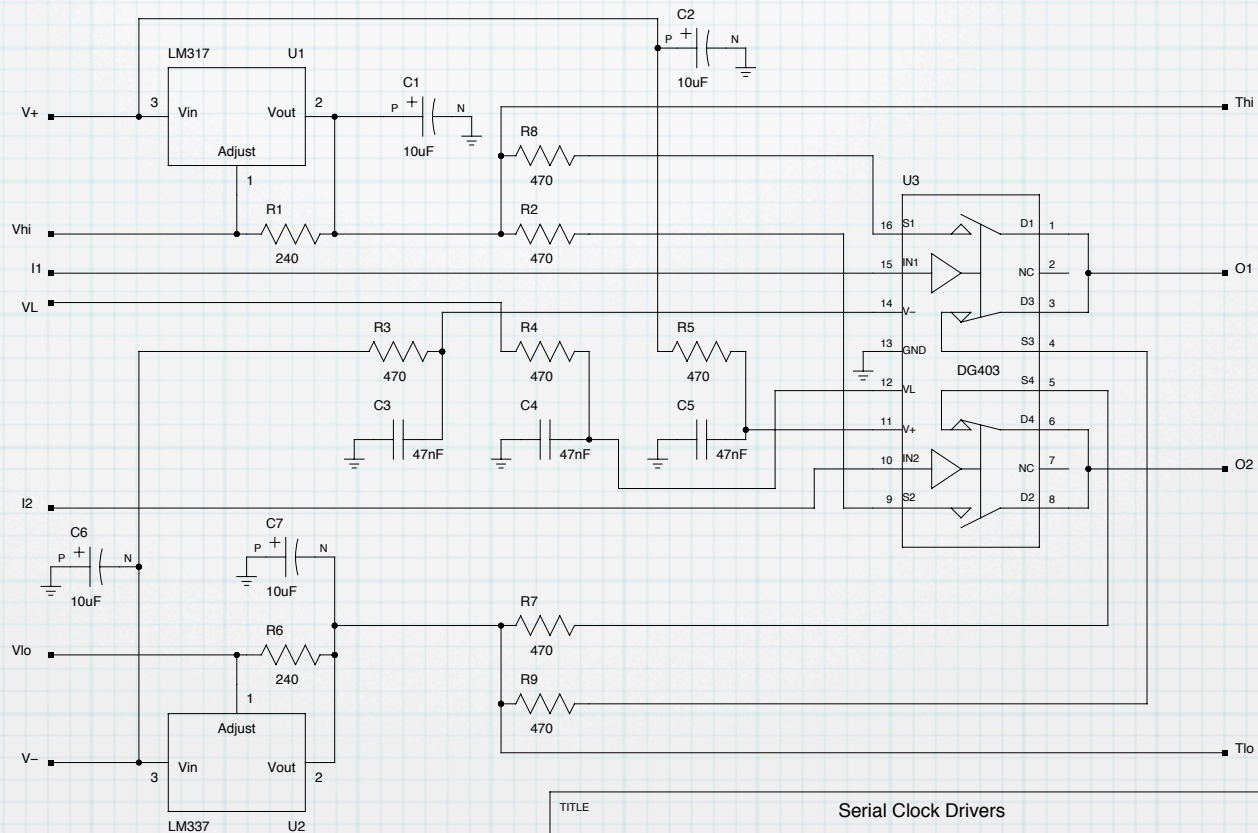 


TITLE		Serial Clock Drivers	
FILE: \$Source: /cvs/Osaka/SXI/Schematic/SerialDrivers.sch.v \$			
DATE	\$Date: 2007/06/08 00:55:28 \$	REVISION:	\$Revision: 1.1 \$
PAGE	1 OF 1	DRAWN BY:	\$Author: jpd \$

 

Operation at 1 MHz, 200 pF loads

 

 

Power Consumption

1 MHz, $\pm 18\text{V}$ supplies, $\pm 12\text{V}$ clocks,
200 pF loads

Static overhead: 180 mW (LM317L and
LM337L)


Dynamic overhead: 130 mW (DG403)

Power due to load current: 350 mW

Possible improvements

More efficient regulators

Reduced voltage requirements

 


Parallel Clock Driver


Noqsi Aerospace, Ltd.

2822 South Nova Road, Pine, Colorado, USA 80470

+1-303-816-2756 jpd@wispertel.net

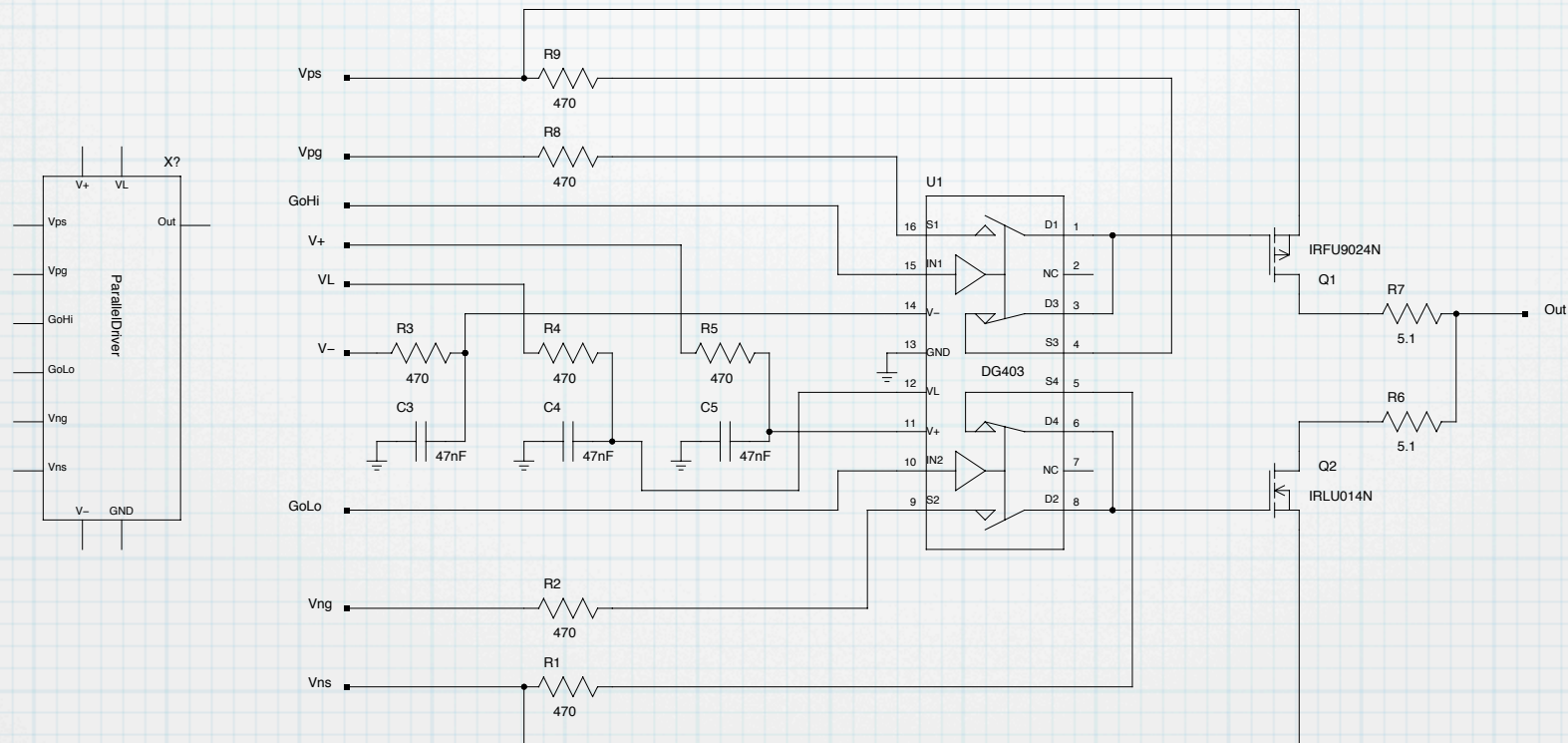

TITLE		Parallel Clock Driver	
FILE: \$Source: /cvs/Osaka/SXI/Schematic/ParallelDriver.sch.v \$			
DATE	\$Date: 2007/06/15 19:36:20 \$	REVISION:	\$Revision: 1.3 \$
PAGE	1 OF 1	DRAWN BY:	\$Author: jpd \$


 


Regulators for Parallel Clocks


Noqsi Aerospace, Ltd.

2822 South Nova Road, Pine, Colorado, USA 80470


+1-303-816-2756 jpd@wispertel.net

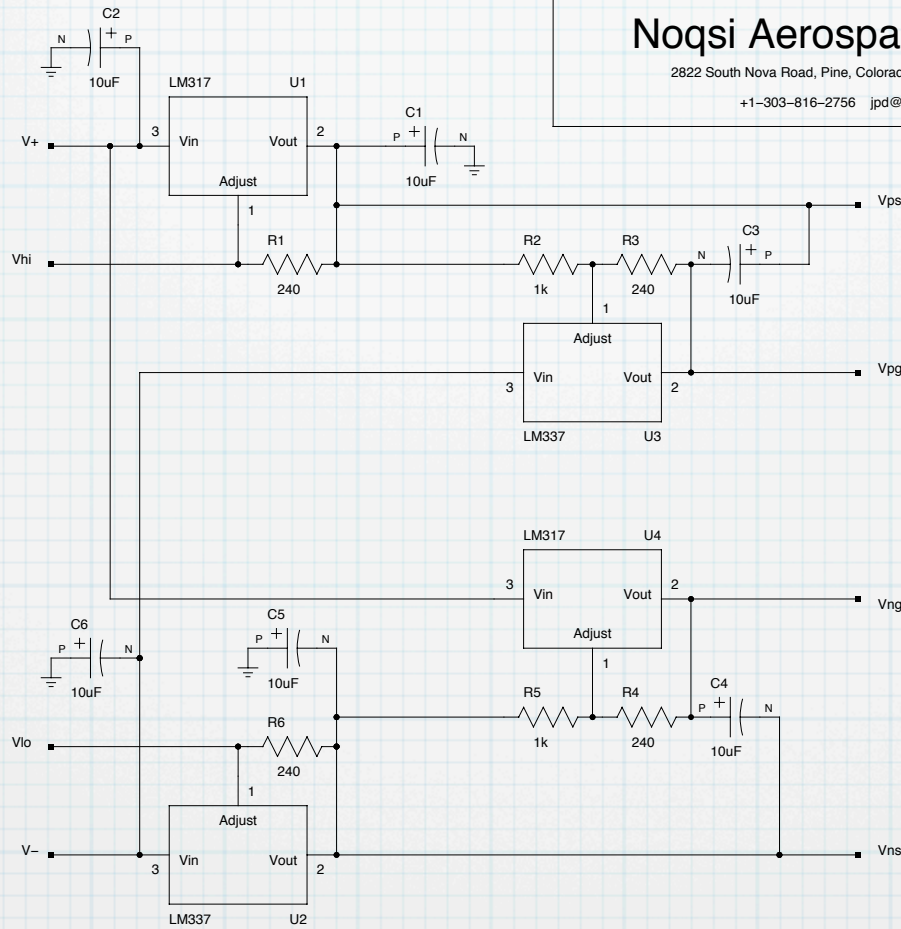 


TITLE		Parallel Clock Regulators	
FILE: \$Source: /cvs/Osaka/SXI/Schematic/ParallelRegs.sch.v \$			
DATE	\$Date: 2007/06/08 22:28:09 \$	REVISION:	\$Revision: 1.2 \$
PAGE	1 OF 1	DRAWN BY:	\$Author: jpd \$

 

Operation at 167 kHz, 78 nF load

 

 

Power Consumption

167 kHz peak, 43 kHz average, $\pm 18V$ supplies, $\pm 12V$ clocks, 78 nF load

Regulators: 540 mW static


Can serve four drivers

Driver dynamic power (one driver):

2.8 W average

11 W peak

99% of this is due to load

 

Discussion of clock power

CCD clock power scales unfavorably with increasing telescope focal length

See SPIE 6266-56 from 2006

Two phase CCD's need large swings

Clock power scales as CV^2


Need to refine requirements versus power

Available power?

Frame store time (streaking)?

Fast modes and pixel summation?

Reduced clock swings?

 

Digital to analog conversion

Two possible approaches:

CMOS resistive ladder DAC's (like ASCA, Suzaku)


This technology tends to be somewhat sensitive to radiation dose.

For recent projects, I've used the AD5621 (tiny, micropower).

Serial oversampling (delta sigma) DAC's (like Suzaku TEC controller).

Somewhat more complicated, but most complication is in FPGA.

 Need extra analog filtration, but that's not difficult.




DAC output amplifier


Noqsi Aerospace, Ltd.

2822 South Nova Road, Pine, Colorado, USA 80470

+1-303-816-2756 jpd@wispertel.net

 

TITLE	Band limited amplifier		
FILE:	SSource: /cvs/Osaka/SXI/Schematic/AlgebraicFilt.sch.v \$		
DATE	\$Date: 2007/06/19 18:26:46 \$	REVISION:	\$Revision: 1.1 \$
PAGE	1 OF 1	DRAWN BY:	\$Author: jpd \$

 

DAC output amplifier

Regardless of DAC technology, need amplifier from ~3V DAC output

Potential noise introduction path

Bandwidth limited

Capacitive output

Power very sensitive to voltage

For supply span <30V, use OP220 (as on ASCA, Suzaku).

But need span of ~36V for ± 15 V clock range.

For larger span, fewer choices. OP77 is maybe best, but takes 20X the current of OP220!



Bias Drivers

Requirements


Output to +25V

Most very low current

Can use DAC output amplifiers directly.

How much current needed for CCD charge amplifier drains?

Can use OP220 here to save power.

 

Video Chains

ASIC based on MD01 is possible

Very small, energy efficient


No “dragon’s teeth”, excellent DNL

Backup plan: Suzaku-like chains

Fast, low power opamps and switches make this approach much easier than 10 years ago

Some “dragon’s teeth” from ADC DNL.

Need requirements, CCD specs

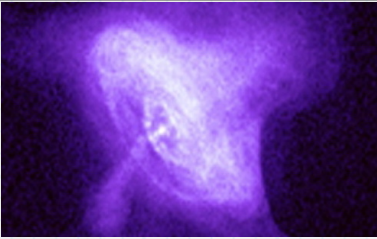

Sequencer

Requirements?

Lots of ways to do this:

- ASCA-like single level state machine

- Suzaku-like multilevel microcode

- Mix and match features from those


- RAM/Flash FPGA's make state machine approach flexible

How much bandwidth/latency to DE/DP?

- On ASCA, DE issued a sequencer command every pixel

- Suzaku DE doesn't work so hard

Who designs this?

 

Temperature Control

Is this required?

And what are the requirements?

If so, who designs this?

Thermal, mechanical, electrical design are all closely connected here.




Interface

FPGA to present AE interface to DE/DP?

SpaceWire?

Other requirements?

Who will design this?

 

Final Questions

When?

Schedule?

Resource budgets (power, mass, ¥, etc.)?

System

System engineering ISAS-like?

Preferred parts?

Preferred interfaces?